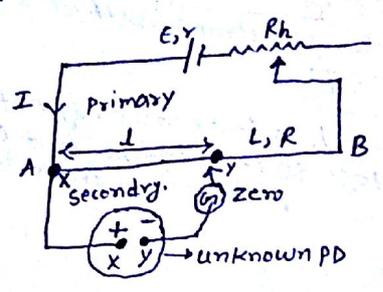


ELECTRICAL MEASURING INSTRUMENT

- Expt
- Current → Galvanometer / Ammeter
 - Voltage → Voltmeter / potentiometer
 - Resistance → meter bridge / post office box
 - Emf of battery / internal resistance → potentiometer.

Potentiometer :-

- * Ideal voltmeter
- * use to measure potential difference.
- * Based on zero deflection method.
- * It is not based on Wheat Stone Bridge.
- * It doesn't draw any current from ckt under measurement so measure accurate value & behave like voltmeter.
- * Its principle based on the concept of that no current will flow b/w two points if points are at the same potential.



11) → Primary cell / ckt

$$I = \frac{E}{R + R_h + r}$$

$$V_{AB} = IR$$

* Potential gradient (x) = potential ↓ unit length of wire

$$L \rightarrow V_{AB}$$

$$l \rightarrow \frac{V_{AB}}{L}$$

$$x = \frac{V_{AB}}{L}$$

12) → Secondary ckt →

→ unknown PD connection in secondary ckt b/w 'X' & 'Y' & balanced length obtained by moving a jockey on potentiometer wire.

If balance length = l

then unknown voltage (V) = $x \cdot l$

13) → Range →

$$\text{Range} = V_{AB} = xL$$

$$\text{Range} \propto x$$


14) → Sensitivity (S) :-

$$S \propto \frac{1}{x}$$

NOTE → Rheostat (Rh) use in primary to adjust (x) so that -

- * x (↑), Range (↑), Sensitivity (↓)
- * x (↓), Range (↓), Sensitivity (↑)

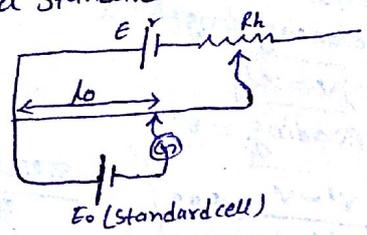15) → Standardisation of potentiometer :- In this process is for finding Aquireate (x) by balancing a standard cell on potentiometer wire.




$$\because E_0 = x \cdot l_0$$

$$x = \frac{E_0}{l_0}$$

Application of potentiometer:

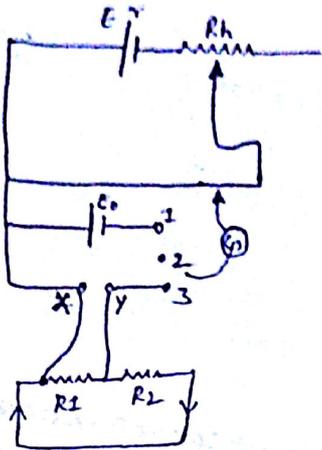
1) → To measure P.D across current carrying Resistance →



1-2 $x = \frac{E_0}{I_0}$

2-3 If balance length = l
 $V R_1 = x l$


2) → To measure EMF of a cell →

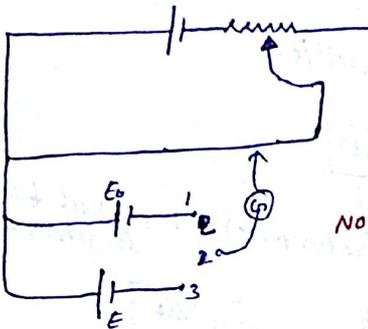

* If we connect 1-2, $x = E_0 / I_0$
 * If we connect 2-3, If balance length = l
 $E = x l$

NOTE → * This balance length is for EMF only not for terminal voltage so it is independent of x.
 * Balance length is independent from internal resistance.

3) → To compare EMF of cell →

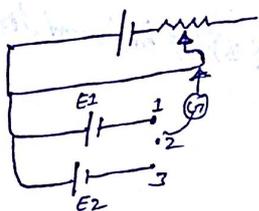


1-2, $E_1 = x l_1$ - (i)
 2-3, $E_2 = x l_2$ - (ii)

(i) $\frac{E_1}{E_2} = \frac{l_1}{l_2}$

NOTE → Standardisation not require.

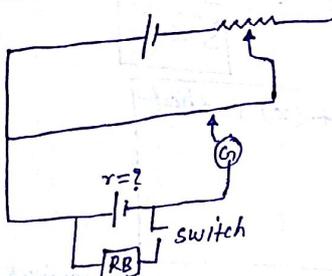4) → To measure internal Resistance of cell →




* Switch off $E = x l_1$
 * Switch on $V = x l_2$

$r = \left(\frac{l_1 - l_2}{l_2} \right) (R_B)$

NOTE → Standardisation Not require.

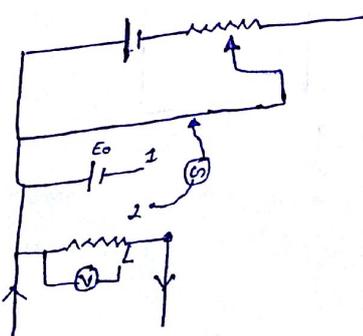5) → Calibration of voltmeter →
 → To find error in voltmeter




1-2 $x = E_0 / l$
 2-3 If balancing length = l
 $V = x l$

If voltmeter Reading = V'

$\% \text{ Error} = \frac{V' - V}{V} \times 100$

$\frac{\text{असुधत} - \text{सुधत}}{\text{सुधत}} \times 100$

161 → calibration of Ammeter →

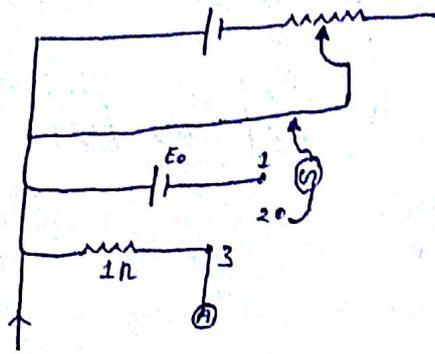

1-2 $x = E_0/I_0$

2-3 $V_{1n} = xI$


$I = xI$

Let (A) Reading = I'

$\% \text{ Error} = \frac{I' - I}{I} \times 100$

Meter Bridge

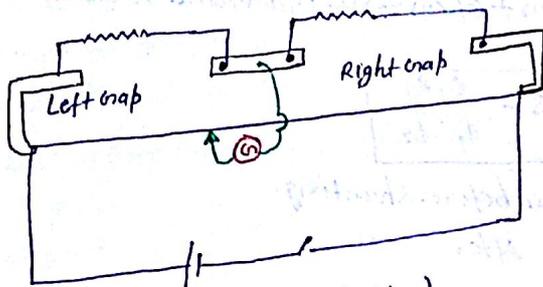- * Based on Wheat stone Bridge.
- * Use to measure Resistance.
- * Based on zero deflection method.
- * unknown resistance is measured by comparing with known Resistance.



In balance condition (null deflection)

$\frac{P}{Q} = \frac{R}{S}$

$S = \left(\frac{100-l}{l}\right) R$


$\frac{l}{100-l} = \frac{R}{S}$

NOTE → * Formula use करना है $\frac{P}{Q} = \frac{R}{S}$
 * Left में 'P' होता है और उसके gap में 'R', Right में 'Q' होता है और gap में 'S' है!
 * फिरता Resistance जगाया तो उसकी wire ki length भी जगाया!

Moving coil Galvanometer :

Deflection \propto current

$\phi \propto I$

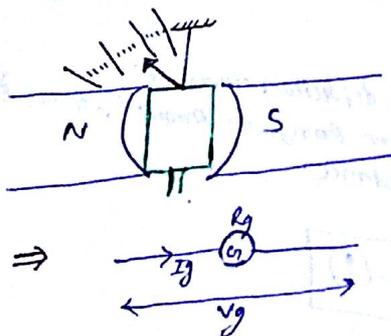

$I_g \Rightarrow$ Full deflection current
 $V_g \Rightarrow$ Full deflection voltage
 $R_g \Rightarrow$ Resistance of galvanometer
 $V_g = I_g R_g$

- * Galvanometer is Ammeter of I_g Range & Voltmeter of V_g Range.
- * Resistance of galvanometer (10 Ω - 1000 Ω)

Current sensitivity (C_s)

Deflection for unit current.

$$I \rightarrow \phi$$

$$1 \rightarrow \frac{\phi}{I}$$

$C_s \rightarrow \frac{\phi}{I}$

Voltage Sensitivity

$$V \rightarrow \phi$$

$$1 \rightarrow \frac{\phi}{V}$$

$$V_s \rightarrow \left[\frac{\phi}{V} \right] \cdot \left[\frac{\phi}{I R_g} \right] = \frac{C_s}{R_g}$$

Figure of merit / anal. const.

It is Inverse of C_s .

$F_M = \frac{1}{C_s} = \frac{I}{\phi}$

Shunting

- Means parallel.
- To apply small Resistance in || of galvanometer.



→ Due to shunting some part of current is deviated to shunt so deflection ϕ is reduced.

→ Required shunt $S = \frac{\phi_2 R_g}{\phi_1 - \phi_2}$

ϕ_1 → deflection before shunting.


ϕ_2 → " After " "

NOTE → * Galvanometer is type of Ammeter also at Range of I_g .
* Galvanometer is type of voltmeter also at Range of V_g .

Ammeter

- Always connected in series.
- Its Resistance is small.
- Resistance of ideal Ammeter is zero.

(G) to (A) conversion → small shunt is applied || to galvanometer.

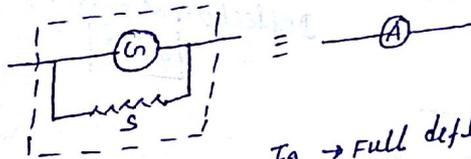

$S = \frac{I_g R_g}{I - I_g}$

I_g → Full deflection current.
 I → Full range of Ammeter (संलग्न I)
 R_g → Resistance.

* $S(\downarrow) \Rightarrow \text{Range}(\uparrow)$

Voltmeter

- Always connected in // to calculate P.D.
- Its Resistance is high
- Resistance of ideal voltmeter is ∞.

(G) to (V) conversion

High Resistance is connected in series with galvanometer.




$$R = \frac{V}{I_g} - R_g$$

V = Required Range of voltmeter

- * $R(I) \Rightarrow (V)$ Range (I)
- * $R(V) \Rightarrow R_g + R$
- * $R_A < R_g < R_V$

colour coding of carbon resistance

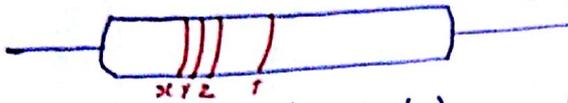

1st three colour (value)

(Black) B-0

(Brown) B-1

R-2

0-3

Y-4

Green → G → 5

Blue → B → 6

V → 7

Grey → G → 8

White → W → 9

Fourth colour

Gold $\pm 5\%$

Silver $\pm 10\%$

$$R = xy \times 10^z \pm T$$